



Smart ByPass


Designed By Erik Vincent

A reliable and professional bypass solution; The Smart ByPass has been designed with a “smart” preprogrammed ATTINY chip at its core and covers almost everything you could want in a bypass solution. This kit comes with all the parts you need (see BOM below) to build the Smart ByPass, including a preprogrammed chip, making its construction for you simply a matter of soldering. Just some of the many features built into the Smart ByPass include:

- Reliable, ‘soft touch’ non-latching SPDT stomp E-Switch (rated at 30,000 cycles)
- Reliability of a relay bypass solution (analogue latching relay)
- Regulated (power filtered) 5v output
- Smarter reverse polarity protection for your pedals using PFETs instead of diodes
- Kit includes Preprogrammed attiny13a and all parts for easy assembly including the footswitch!
- The state of the relay is held for ~1/2 a second if power is disconnected. This is to prevent slight power interruptions that would otherwise cause the Smart Bypass relay to switch to bypassed mode.


Bill of materials

Relay		Capacitor	
L1	TQ2-L-5V	C1	1uf (film)
		C2	1uf (film)
Stomp Switch		C3	100nf (film)
	Mini Non-Latching SPDT Stomp Switch		
IC		Transistor	
U1	LP2950-50LPRE3 (68MR7CE)	Q1	VP2106N3-G
U2	ATTINY13A-PU		
U3	G3VM-351A	Resistor	
		R1	1k5
LED		R2	1k5 (LED CLR)
LED1	5mm Status LED	R3	10k

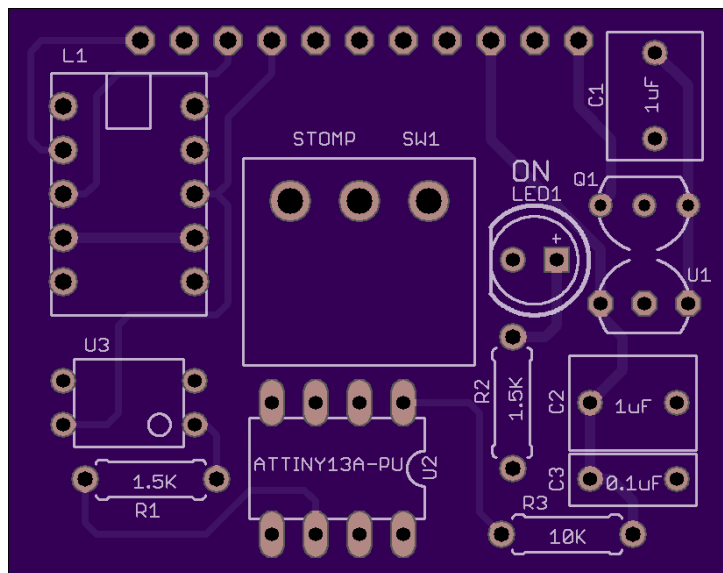


Assembly / Soldering

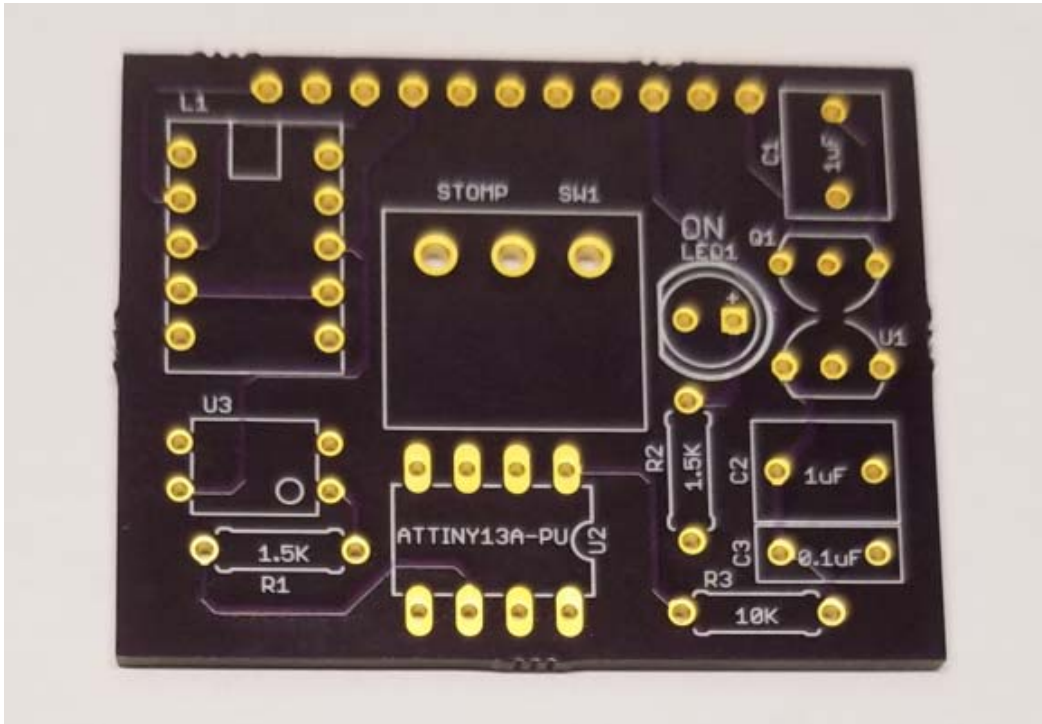
1. This is the top of the Smart ByPass PCB.



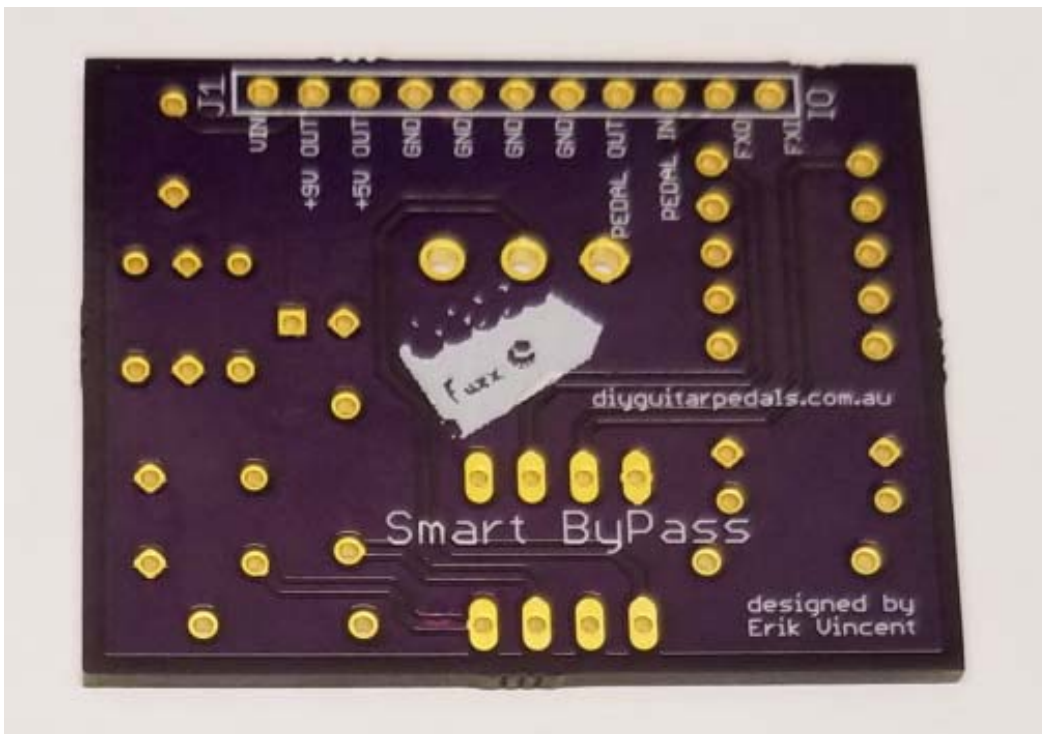
2. This is the bottom of the PCB. Note the J1 Header



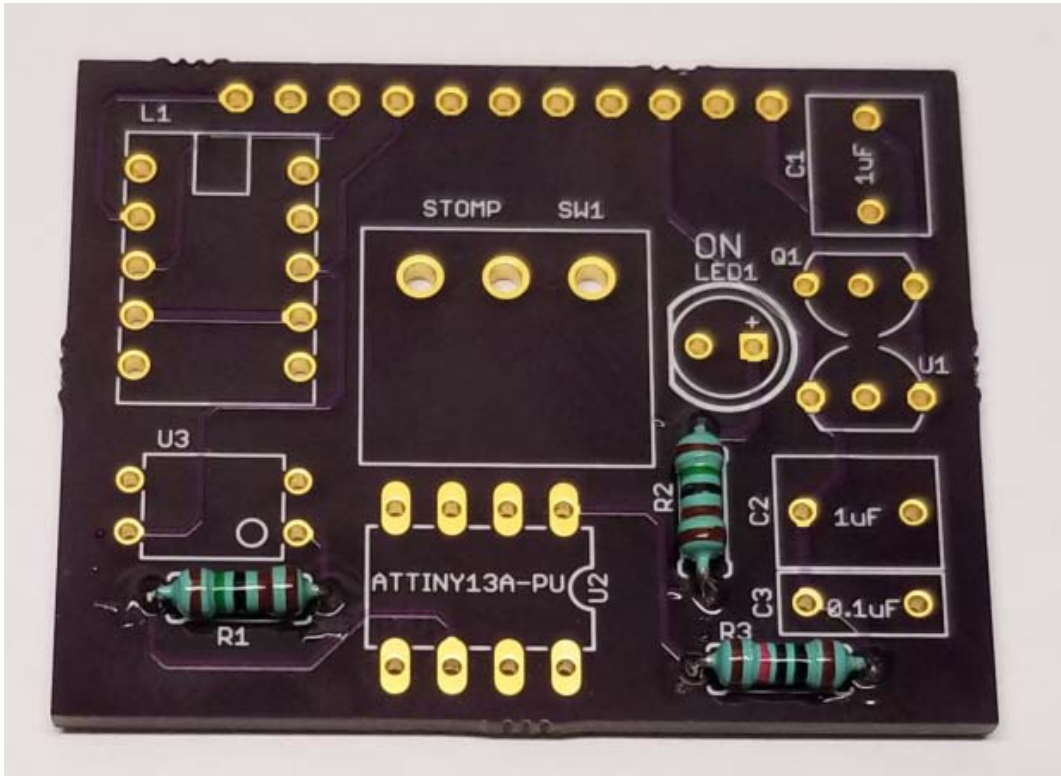
3. First, solder the 1/4W resistors. The values for R1 and R2 are 1.5K. The value of R3 is 10K.



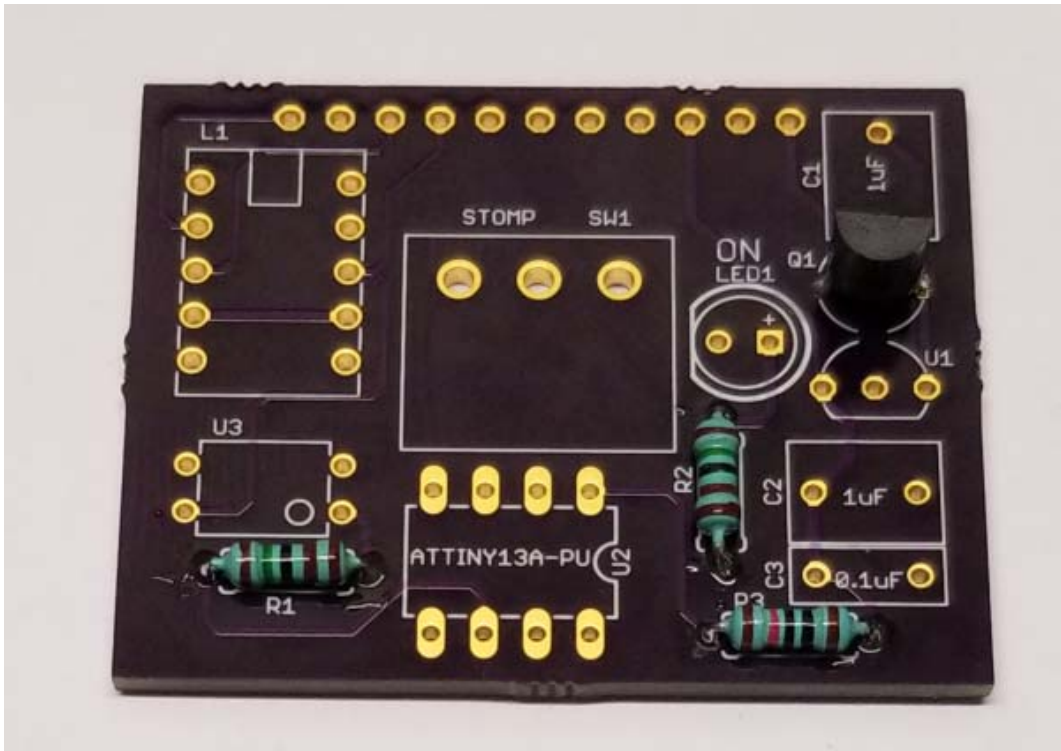
4. Next, solder the P-Channel MOSFET, Q1.




5. Next, solder the 5V Regulator, U1.

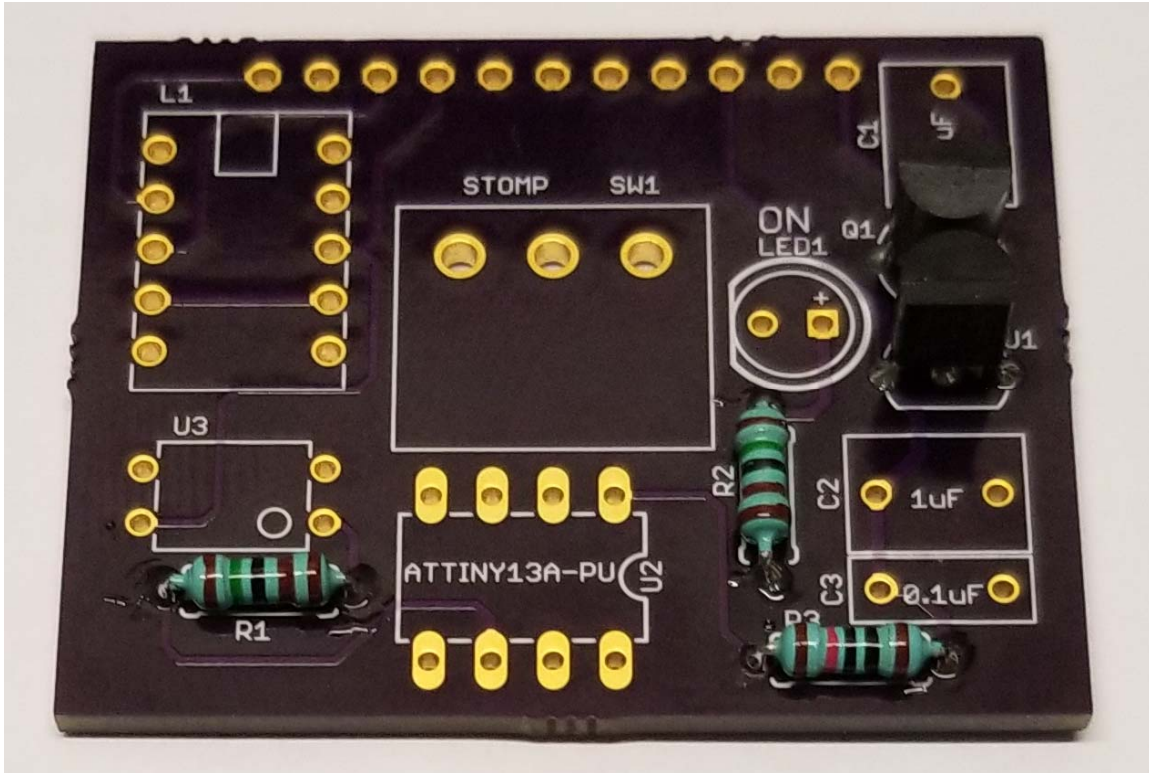

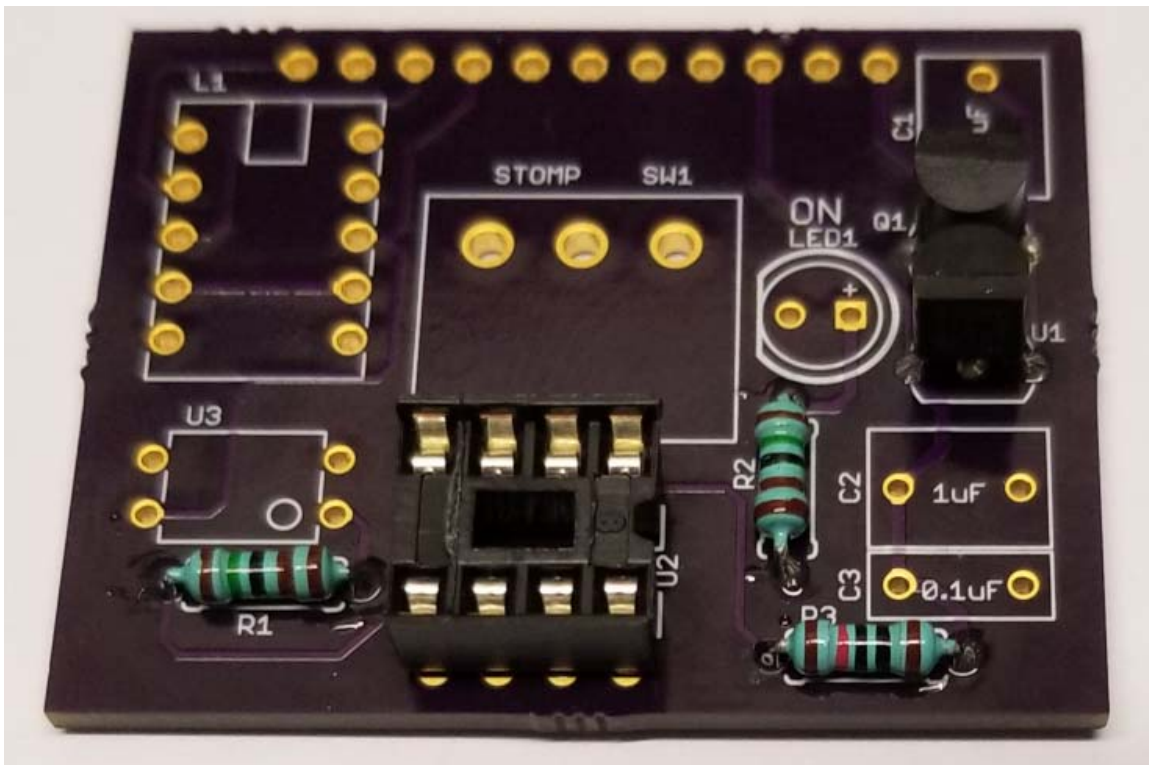
6. Next, solder the 8-Pin socket onto U2. Let Bono and the Edge know.



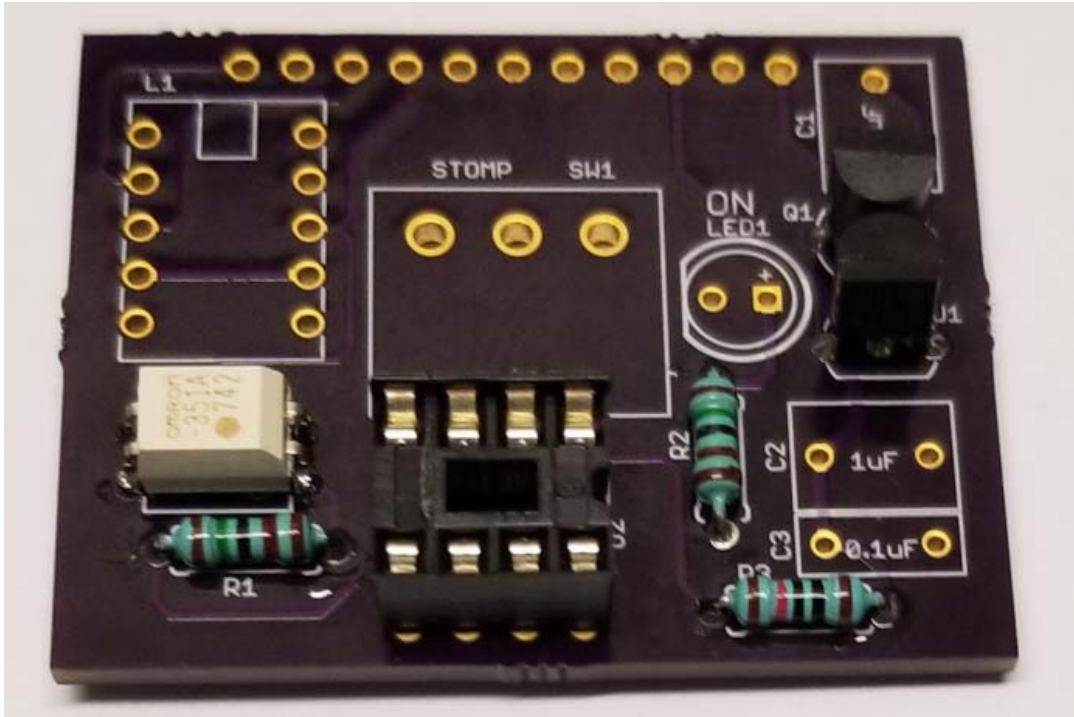
7. Next, solder the solid-state relay, U3



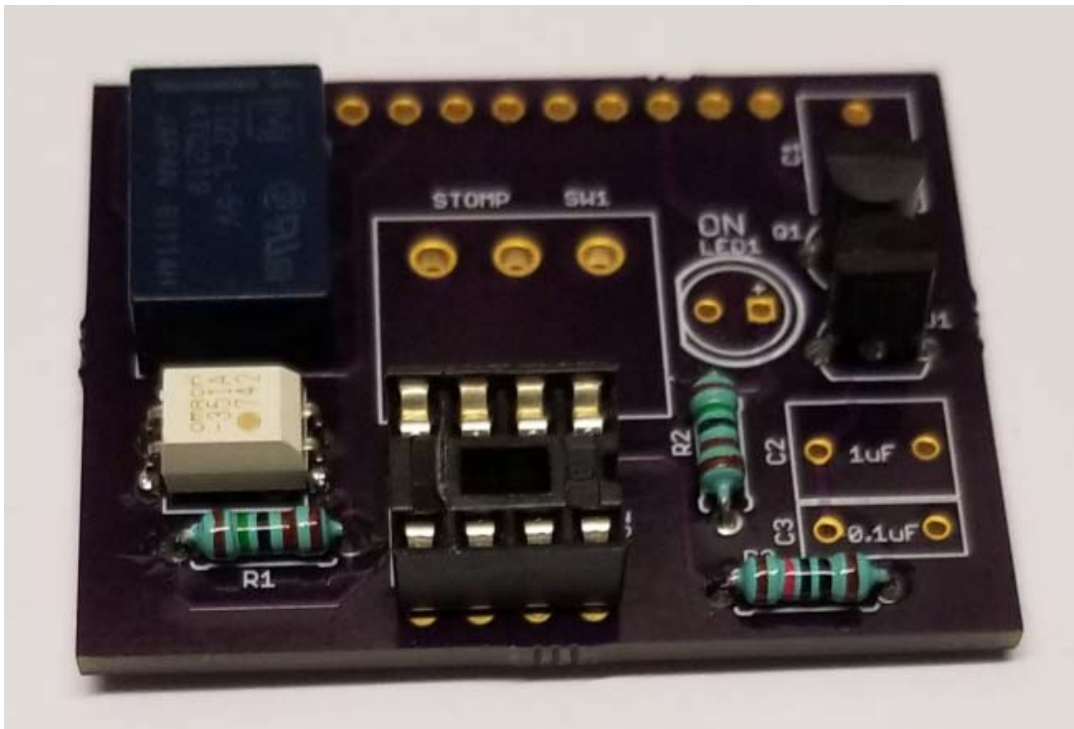
8. Next, solder the small current latching relay, L1



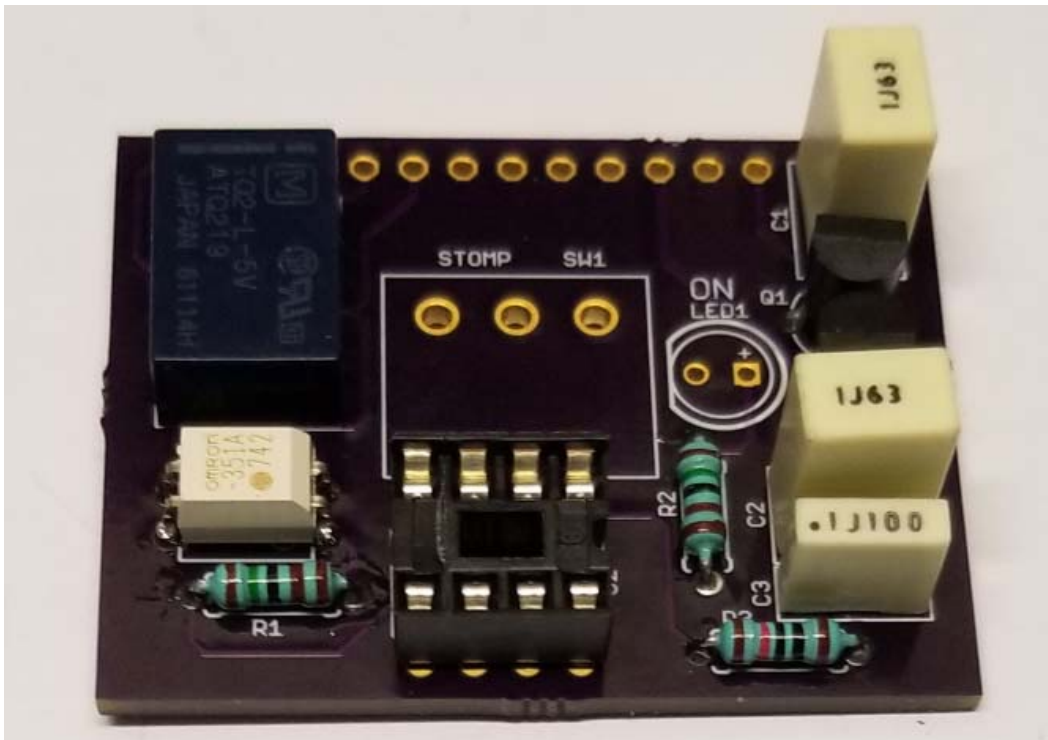
9. Next, solder the film capacitors, first with C3, then C1 and C2. The values of C1 and C2 are 1uF. The value of C3 is 0.1uF



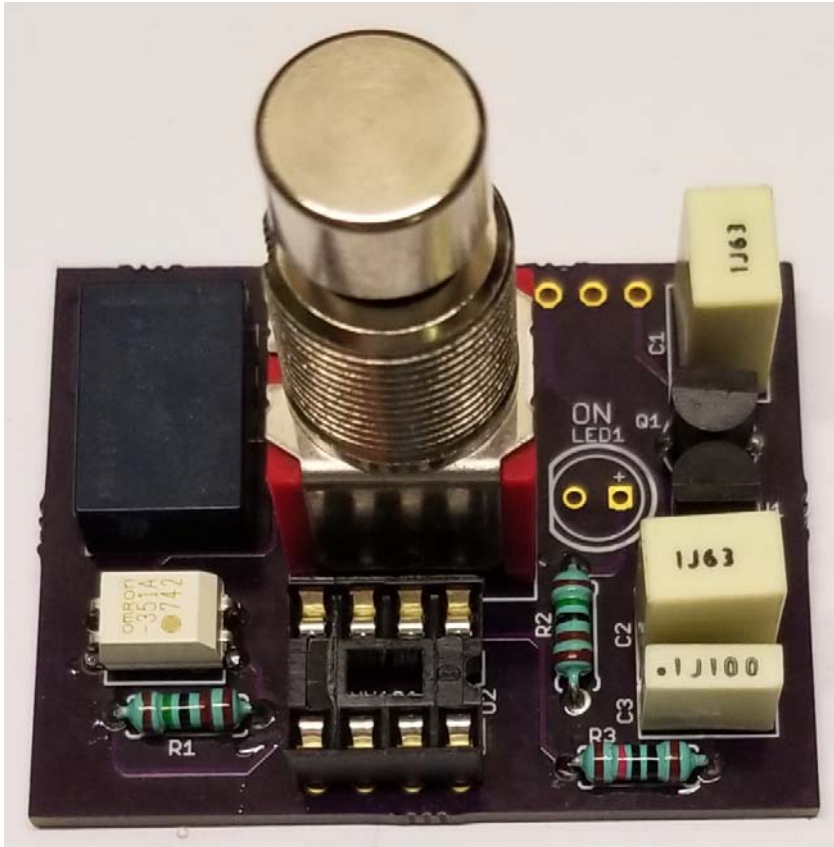
10. Next, solder up the stomp switch to SW1



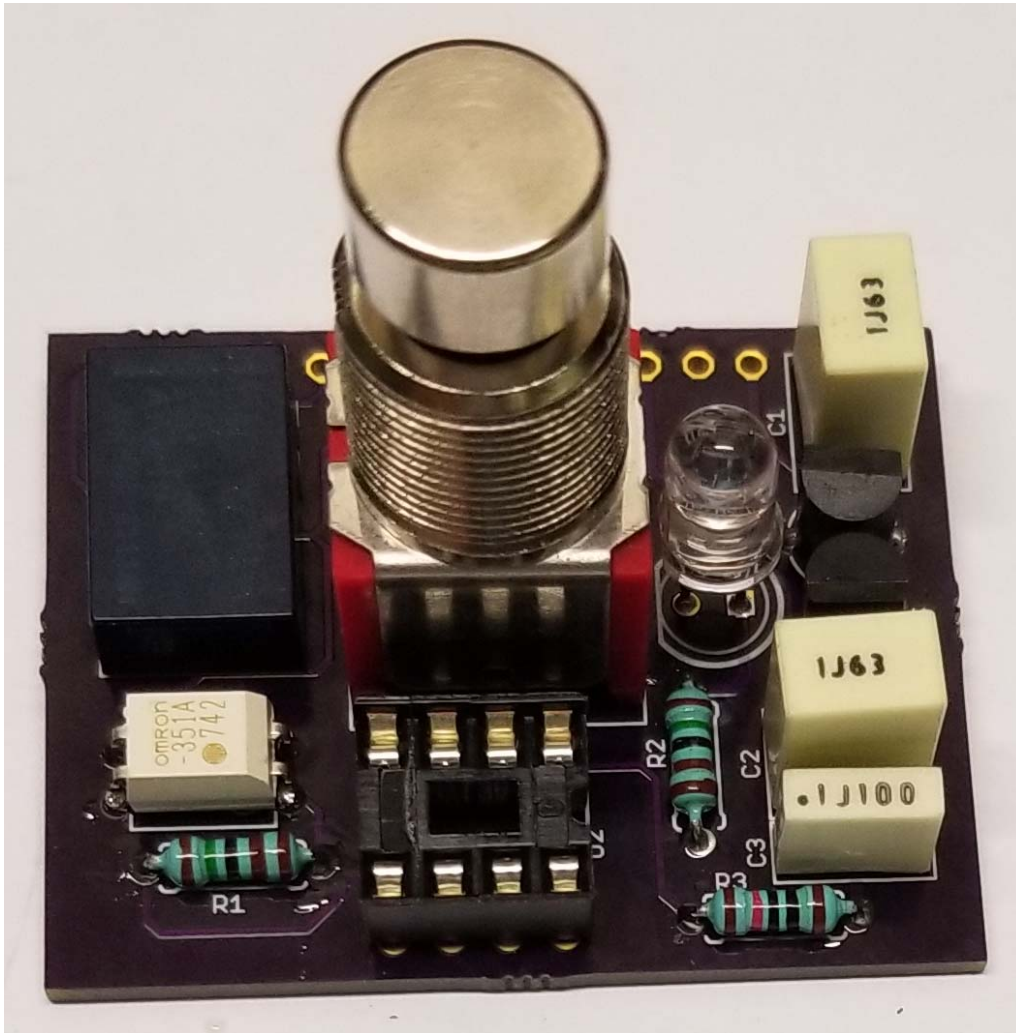
11. Next, solder the LED to LED1. It should stand off a little bit as to get it closer to where the stomp switch will be flush-mounted to the box of the pedal. **Note** the close proximity of the LED, you may need to adjust the position of the led if you are using a 14mm washer.



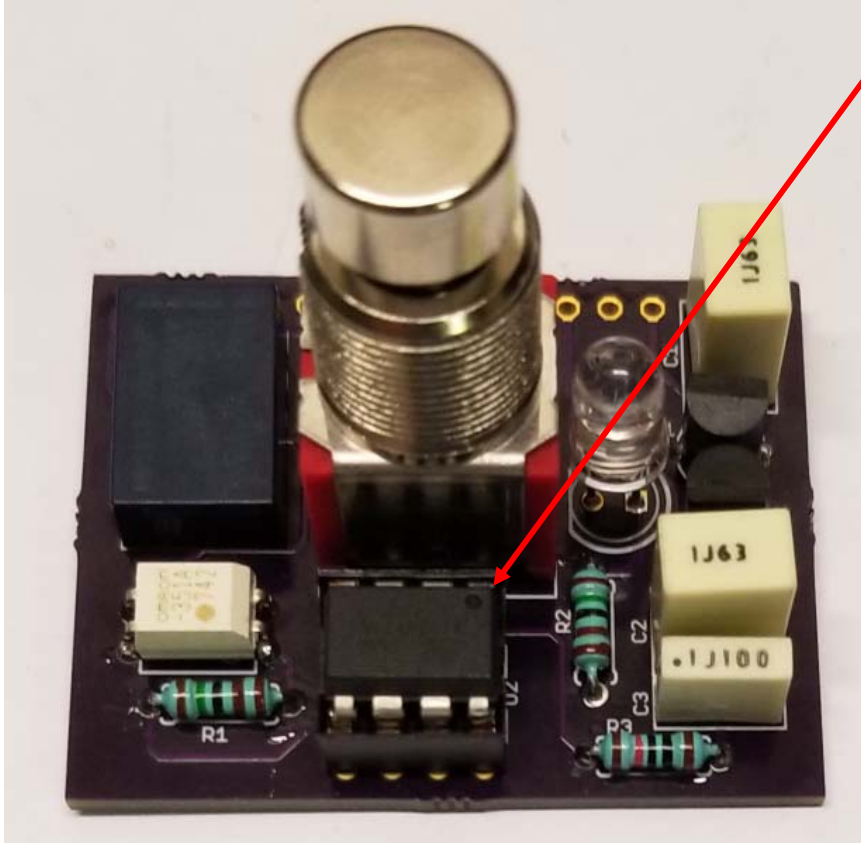12. Next, insert the programmed microcontroller. Make sure the markings are correct.



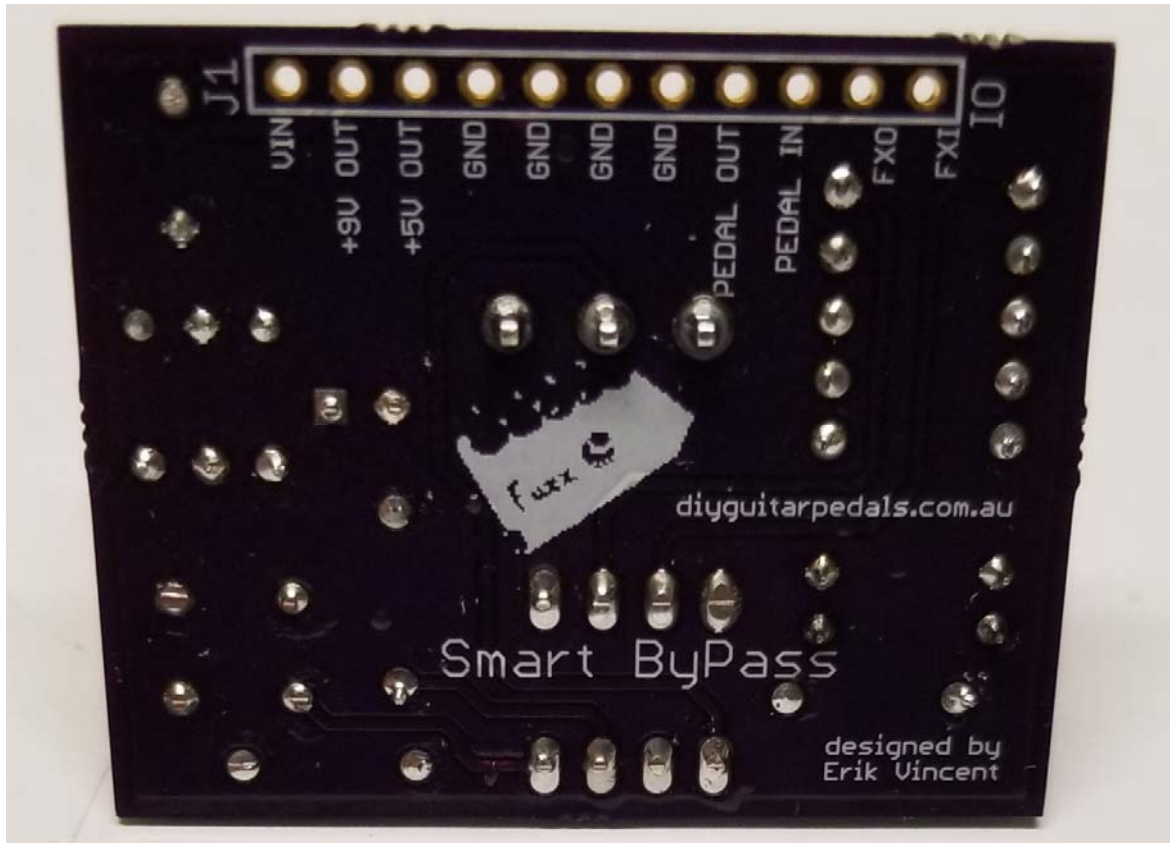13. Flip over to the bottom and note J1 and its labels.



J1 – Header connections

VIN – 9V coming in from battery or wall power

+9V OUT – protected 9V power. This connects to your effect board to provide it 9V power

+5V OUT – protected 5V power up to 100mA. This goes to your effect board if it needs 5V power


GND – this is for common ground components such as power ground, input/output jack ground, and effect board ground. Note, not all grounds may be utilized.

PEDAL OUT – this connects to the output jack's output signal wire

PEDAL IN – this connects to the input jack's input signal wire

FXO – this connects to the effect board's output

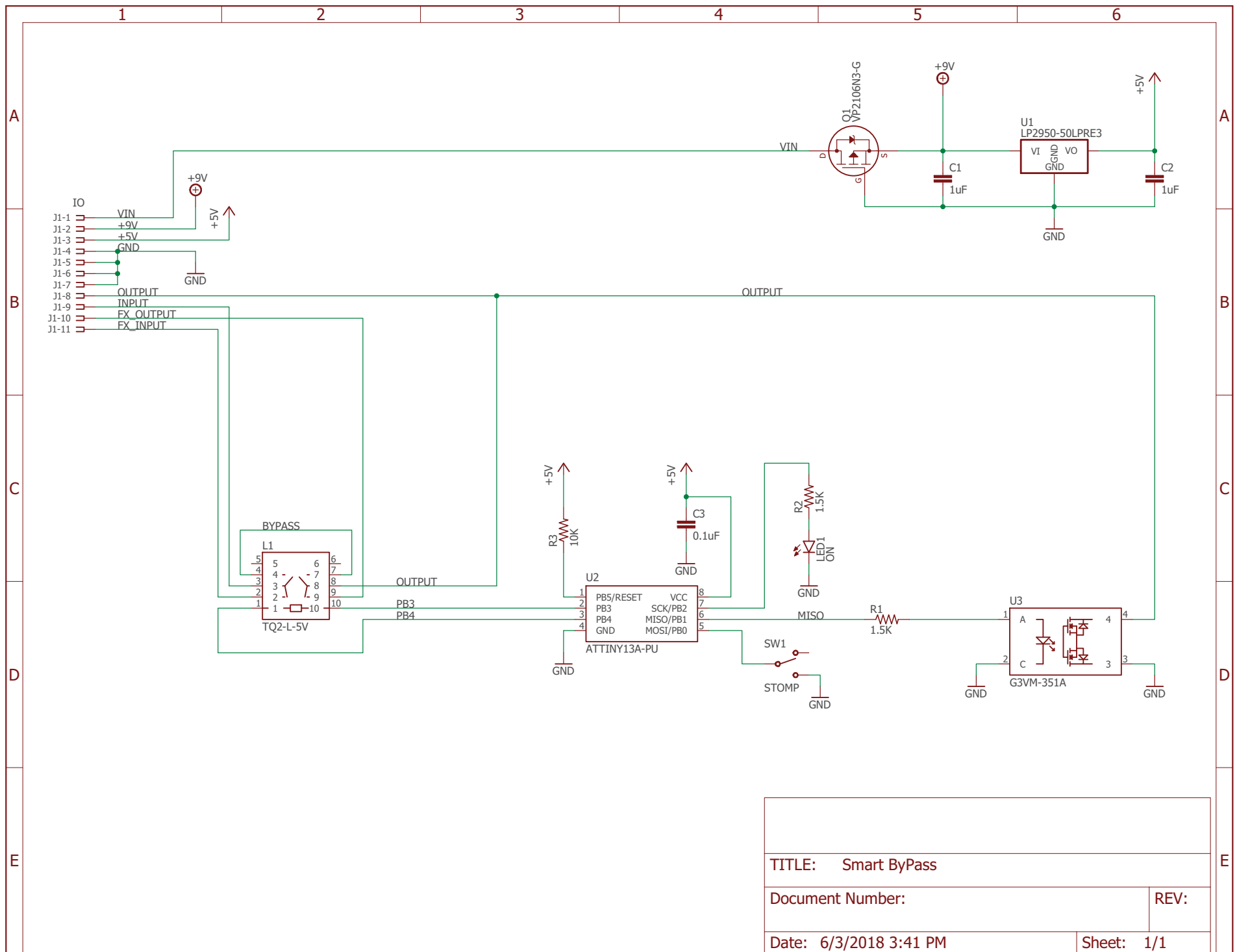FXI – this connects to the effect board's input



TITLE: Smart Bypass	
Document Number:	REV:
Date: 6/3/2018 3:41 PM	Sheet: 1/1