




## Big Knob

What do you get when a One Knob Fuzz collides with a Big Muff Pi Tone Stack? Ok, minds out of the gutter...The Big Knob of course! I've always felt the One Knob Fuzz could use a tone control for versatility as well as experimentation. The Big Muff Pi won the deal, it marries seamlessly with the One Knob Fuzzes expressive output. 16mm pot spacing and silicon transistors make this project a good contender for a silicon fuzz with "bang for buck".

### Bill of materials

Resistors		Capacitors	
R1	1M	C1	100nf
R2	10k	C2	220pf
R3	82R	C3	10nf
R4	2k2	C4	10uf
R5	150k	C5	22nf
R6	1k	C6	220nf
R7	39k	C7	220nf
R8	47k		
R9	430k	Transistors	
R10	100k	Q1	2n3904 (see notes)
R11	15k	Q2	2n3904 (see notes)
R12	3k3	Q3	2n5088
Potentiometer		Diodes	
Volume	100ka (16mm)	D1	1n4001
Tone	100kb (16mm)		

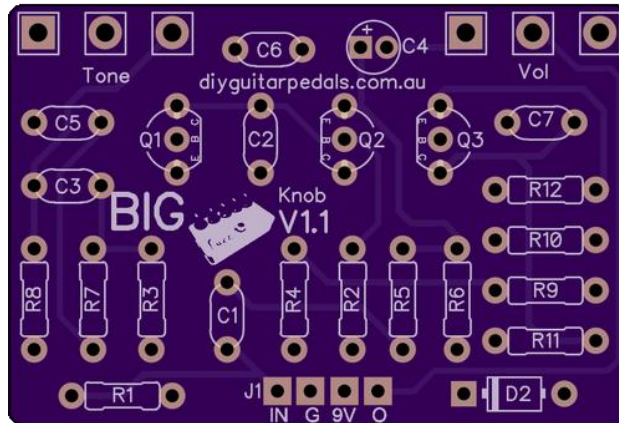

### PCB Spacing

The Big Knob PCB is spaced for 1590B sized enclosures or larger

### Pot Spacing

The Big Knob's pcb mounted potentiometers are spaced for Alpha 16mm potentiometers.

## Modifications

Following is a couple of worthwhile modifications that I discovered experimenting with the Big Knob

### Transistors

This ones obvious. Q1 and Q2 form the gain stages of this silicon fuzz. Increasing and decreasing the gains of these transistors will effect the tonal character of the fuzz. In my experimentation a lot of NPN's sounded good, I personally preferred the S9013's though (available on my store) as they are relatively low gain. To intention mismatch gains (like a lot of fuzzes have), a 2n3904 in Q1 and a higher gain transistor in Q2 may increase sustain of the effect. The original circuit used BC107 and BC108 for Q1 and Q2 respectively, these can still be sourced. Q3 is the recovery stage of the big muff and wont have much effect on tone shaping.

### Germanium Transistor Mod

As this circuit is very similar in topology to the classic circuit of the fuzz face germanium transistors can be used in place of silicons. Note that you will need NPN germanium transistors (PNP's will not work). I have tried low gain NPN's (60 and 80 hfe) and they sound very good. See the sound demo of the Big Knob for an example.

## Shopping List

Although I do not stock all components you will need for the Big Knob, a lot of what you need can be found on my store. The remaining parts you will need are an enclosure (1590b), A 3pdt footswitch, led and current limit resistor and bezel, the 2 potentiometers and any other aesthetic additions you choose.


Click on the value to go to the webstore page:

### Big Knob V1.1 – Shopping List

Resistors		Capacitors	
R1	<a href="#">1M</a>	C1	<a href="#">100nf</a>
R2	<a href="#">10k</a>	C2	<a href="#">220pf</a>
R3	<a href="#">82R</a>	C3	<a href="#">10nf</a>
R4	<a href="#">2k2</a>	C4	<a href="#">10uf</a>
R5	<a href="#">150k</a>	C5	<a href="#">22nf</a>
R6	<a href="#">1k</a>	C6	<a href="#">220nf</a>
R7	<a href="#">39k</a>	C7	<a href="#">220nf</a>
R8	<a href="#">47k</a>		
R9	<a href="#">430k</a>		
R10	<a href="#">100k</a>		
R11	<a href="#">15k</a>		
R12	<a href="#">3k3</a>		
Hardware (for DC power Only)		Transistors	
		Q1	<a href="#">2n3904</a> or <a href="#">S9013</a> (see notes)
		Q2	<a href="#">2n3904</a> or <a href="#">S9013</a> (see notes)
		Q3	<a href="#">2n5088</a>
Hardware (for DC power Only)		Diodes	
	<a href="#">Mini Mono Jack</a> x 2	D1	<a href="#">1n4001</a>
	<a href="#">Compact DC jack - Economy</a>		
	<a href="#">All knobs on my page will fit spacing</a>		
	<a href="#">Wire</a>		

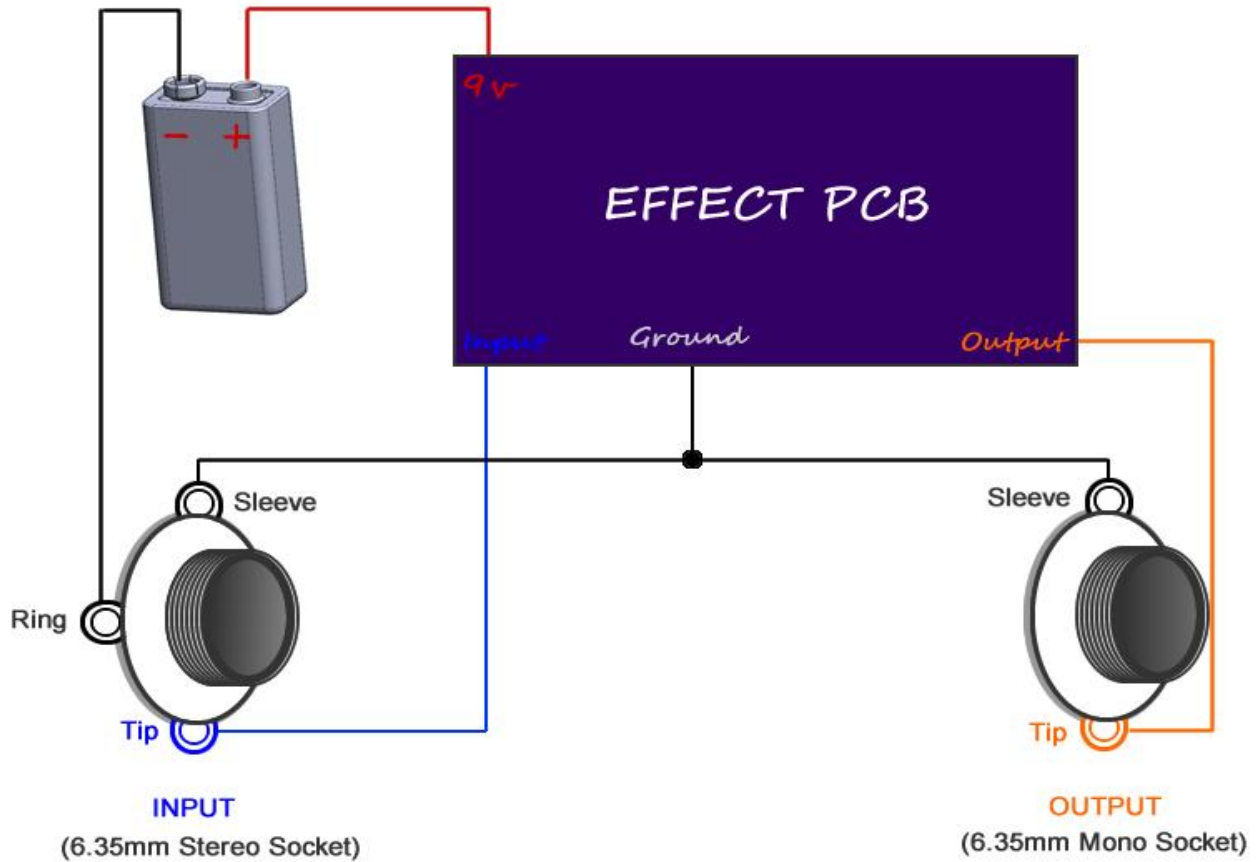
# Testing Your Effect

Using alligator clips or soldering directly, wire your effect as in the following...



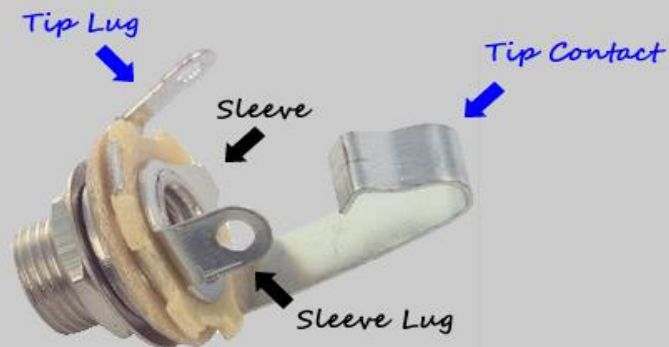
## Input and Output Sockets

Pay close attention to the lugs of your sockets. Look at them side on so that you can distinguish the sockets individual layers. For instance the tip lug is connected to tip contact. The stereo jack looks the same as the socket below except it has an extra lug and contact for "Ring".



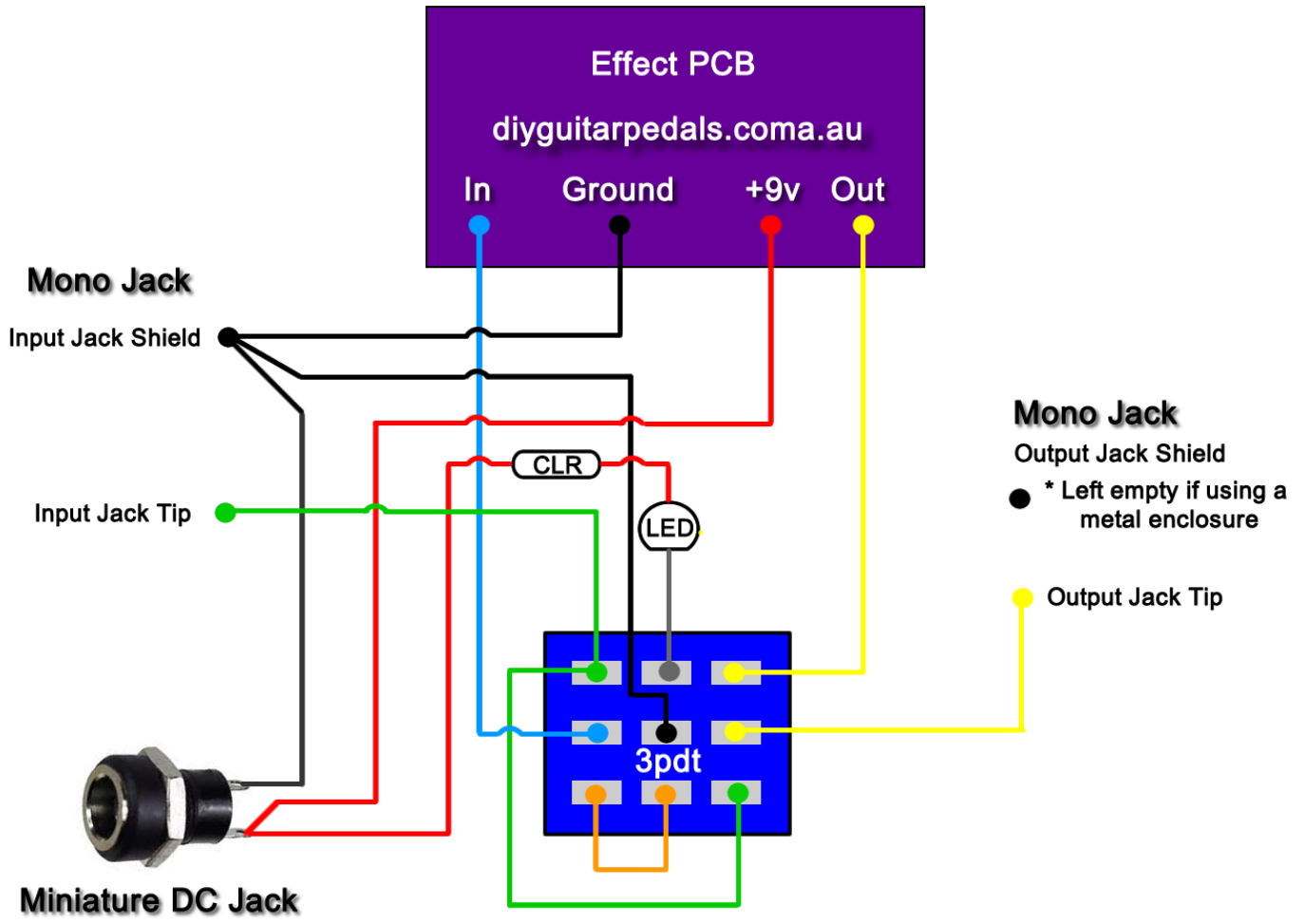
# Offboard Wiring Diagram


Using a non-switched Miniature DC Jacks and 2 Mono Jacks



## 1590b Drill Guide

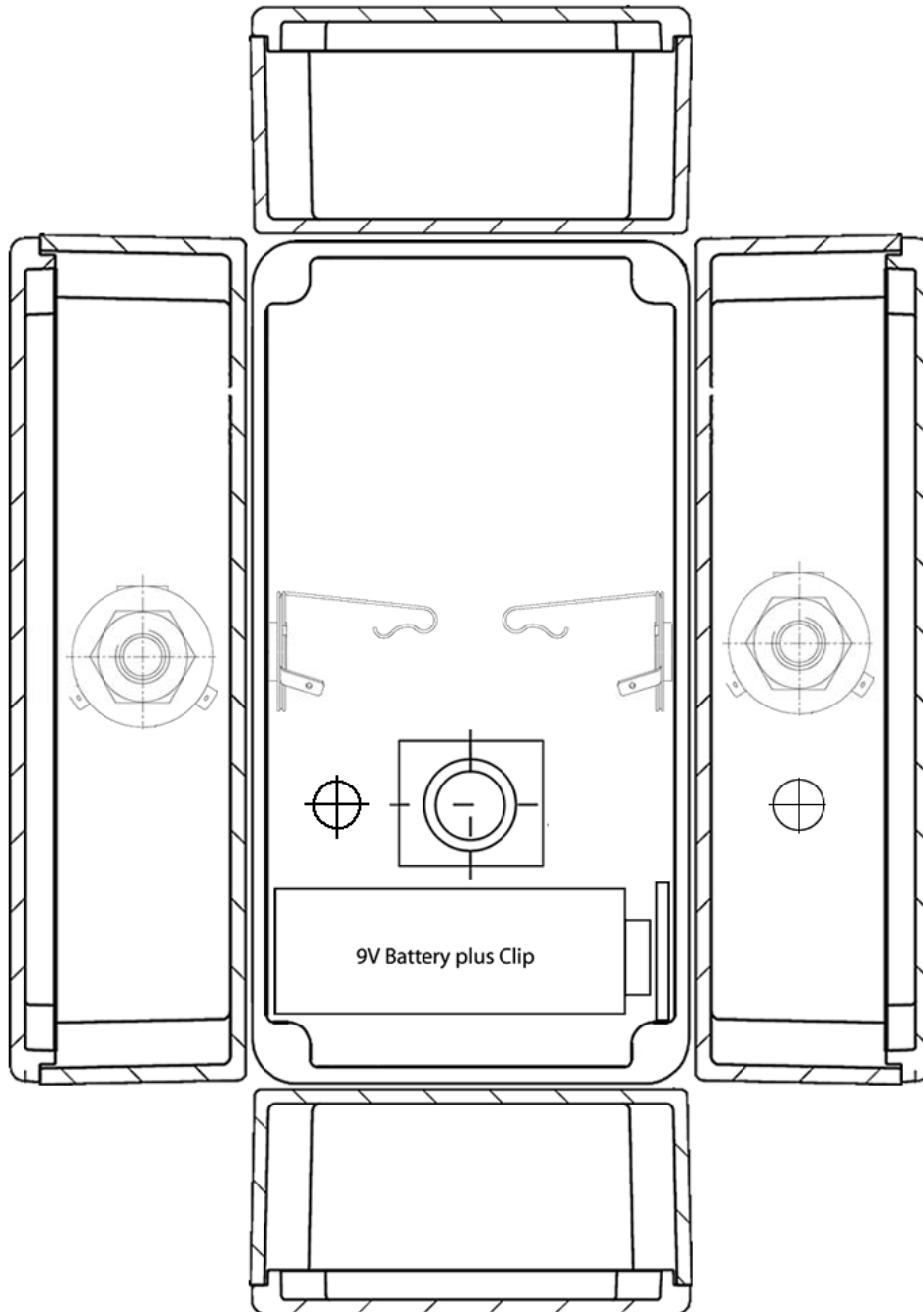

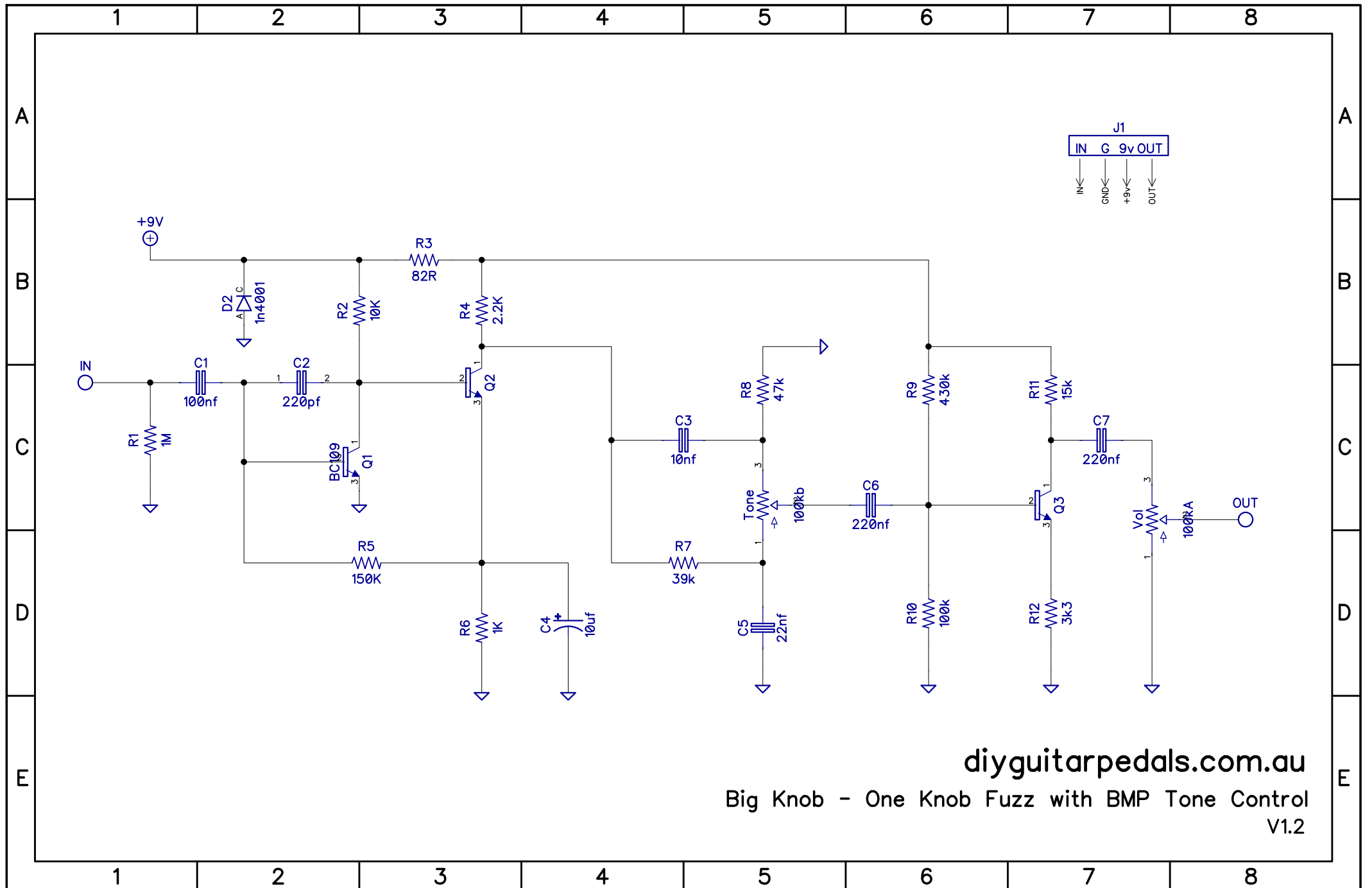due to variances in hardware and enclosure sizes  
please use this template as a guide only  
Please check dimensions before committing to drilling



diyguitarpedals.com.au

Big Knob - One Knob Fuzz with BMP Tone Control

V1.2