




## Big Knob

What do you get when a One Knob Fuzz collides with a Big Muff Pi Tone Stack? Ok, minds out of the gutter...The Big Knob of course! I've always felt the One Knob Fuzz could use a tone control for versatility as well as experimentation. The Big Muff Pi won the deal, it marries seamlessly with the One Knob Fuzzes expressive output. 16mm pot spacing and silicon transistors make this project a good contender for a silicon fuzz with "bang for buck".

### Bill of materials

Resistors		Capacitors	
<b>R1</b>	1M	<b>C1</b>	100nf
<b>R2</b>	10k	<b>C2</b>	220pf
<b>R3</b>	82R (see notes)	<b>C3</b>	10nf
<b>R4</b>	2k2	<b>C4</b>	10uf
<b>R5</b>	150k	<b>C5</b>	22nf
<b>R6</b>	1k	<b>C6</b>	220nf
<b>R7</b>	39k	<b>C7</b>	220nf
<b>R8</b>	47k		
<b>R9</b>	430k	Transistors	
<b>R10</b>	100k	<b>Q1</b>	2n3904 (see notes)
<b>R11</b>	15k	<b>Q2</b>	2n3904 (see notes)
<b>R12</b>	3k3	<b>Q3</b>	2n5088
Potentiometer		Diodes	
<b>Volume</b>	100ka (16mm)	<b>D1</b>	1n4001
<b>Tone</b>	100kb (16mm)		

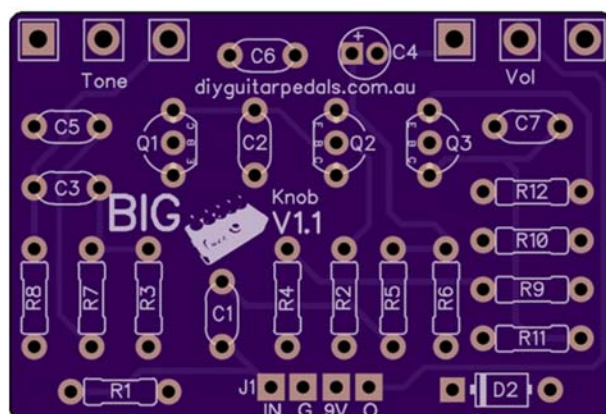

### PCB Spacing

The Big Knob PCB is spaced for 1590B sized enclosures or larger

### Pot Spacing

The Big Knob's pcb mounted potentiometers are spaced for Alpha 16mm potentiometers.

## Modifications

Following is a couple of worthwhile modifications that I discovered experimenting with the Big Knob

### Transistors

This ones obvious. Q1 and Q2 form the gain stages of this silicon fuzz. Increasing and decreasing the gains of these transistors will effect the tonal character of the fuzz. In my experimentation a lot of NPN's sounded good, I personally perferred the S9013's though (available on my store) as they are relatively low gain. To intension mismatch gains (like a lot of fuzzes have), a 2n3904 in Q1 and a higher gain transistor in Q2 may increase sustain of the effect. The original circuit used BC107 and BC108 for Q1 and Q2 respectively, these can still be sourced. Q3 is the recovery stage of the big muff and wont have much effect on tone shaping.

### R3

For most settings the Big Muff Tone Stack should be at unity or greater. However as the big muff pi is so reknowned for sucking the volume out of your signal you could consider socketing R3 and increasing its value for more output volume. Resistor R3 controls the voltage to the collector of Q2 as well as the lpb1 style recovery stage booster on the output. Replacing this resistor with a higher value can have an effect on the biasing of the circuit. A 1k trimpot could be used for adjustment. Be warned a significant volume increase will occur when the trimpot is cranked.

## Shopping List

Although I do not stock all components you will need for the Big Knob, a lot of what you need can be found on my store. The remaining parts you will need are an enclosure (1590b), A 3pdt footswitch, led and current limit resistor and bezel and any other aesthetic additions you choose.


Click on the value to go to the webstore page:

### Big Knob V1.1 – Shopping List

Resistors		Capacitors	
R1	<a href="#">1M</a>	C1	<a href="#">100nf</a>
R2	<a href="#">10k</a>	C2	<a href="#">220pf</a>
R3	<a href="#">82R</a> or <a href="#">1K Trimmer</a> (see notes)	C3	<a href="#">10nf</a>
R4	<a href="#">2k2</a>	C4	<a href="#">10uf</a>
R5	<a href="#">150k</a>	C5	<a href="#">22nf</a>
R6	<a href="#">1k</a>	C6	<a href="#">220nf</a>
R7	<a href="#">39k</a>	C7	<a href="#">220nf</a>
R8	<a href="#">47k</a>		
R9	<a href="#">430k</a>		
R10	<a href="#">100k</a>		
R11	<a href="#">15k</a>	Q1	<a href="#">2n3904</a> or <a href="#">S9013</a> (see notes)
R12	<a href="#">3k3</a>	Q2	<a href="#">2n3904</a> or <a href="#">S9013</a> (see notes)
		Q3	<a href="#">2n5088</a>
<b>Hardware (for DC power Only)</b>		<b>Diodes</b>	
	<a href="#">Mini Mono Jack</a> x 2	D1	<a href="#">1n4001</a>
	<a href="#">Compact DC jack - Economy</a>		
	<a href="#">All knobs on my page will fit spacing</a>		
	<a href="#">Wire</a>		

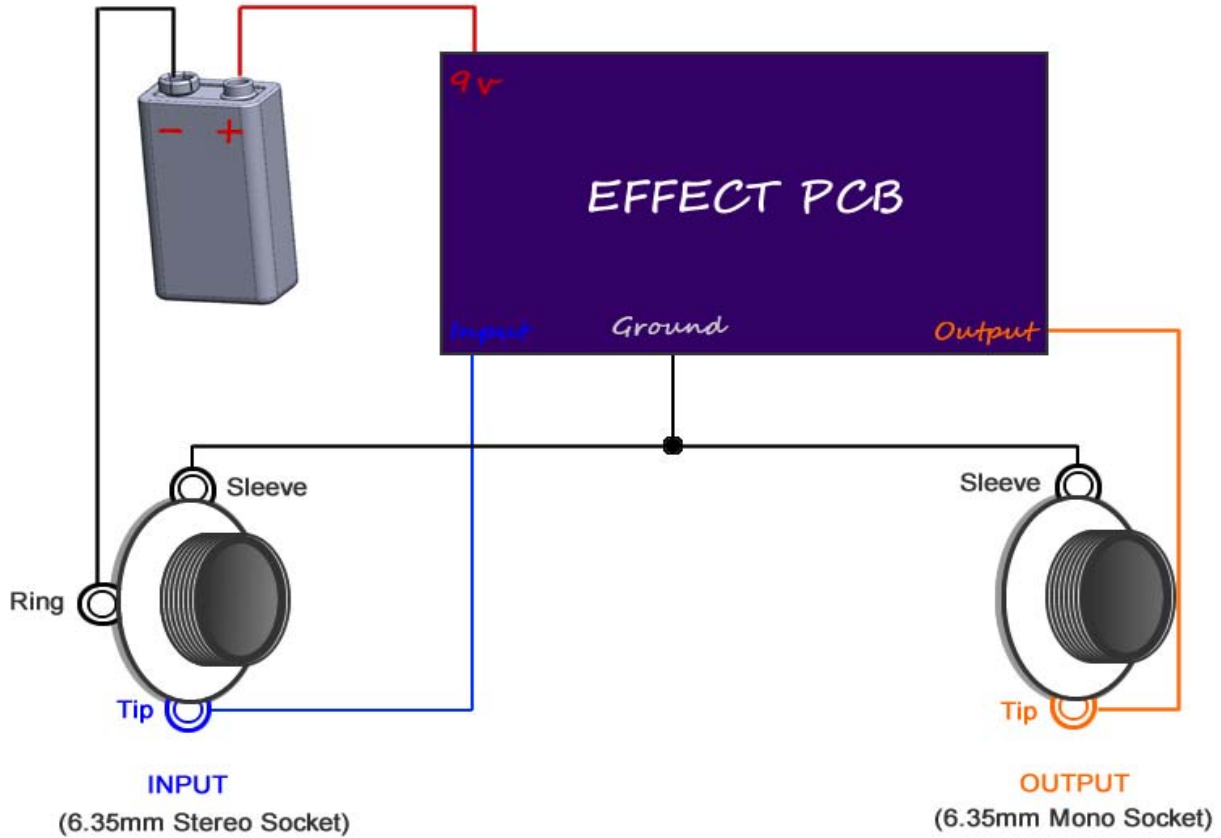
# Testing Your Effect

Using aligator clips or soldering directly, wire your effect as in the following...


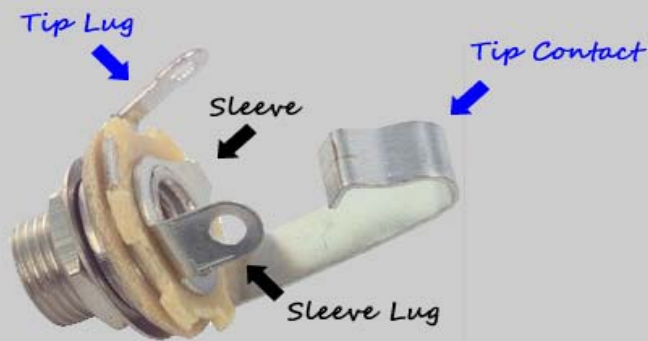
## Input and Output Sockets

Pay close attention to the lugs of your sockets. Look at them side on so that you can distinguish the sockets individual layers. For instance the tip lug is connected to tip contact. The stereo jack looks the same as the socket below except it has an extra lug and contact for "Ring".



# Offboard Wiring Diagram

Using a non-switched Miniature DC Jacks and 2 Mono Jacks

